



WEST BENGAL STATE UNIVERSITY

B.Sc. Honours 3rd Semester Examination, 2019

ELSACOR05T-ELECTRONICS (CC5)

Time Allotted: 2 Hours


Full Marks: 40

*The figures in the margin indicate full marks.**Candidates should answer in their own words and adhere to the word limit as practicable.**All symbols are of usual significance.*

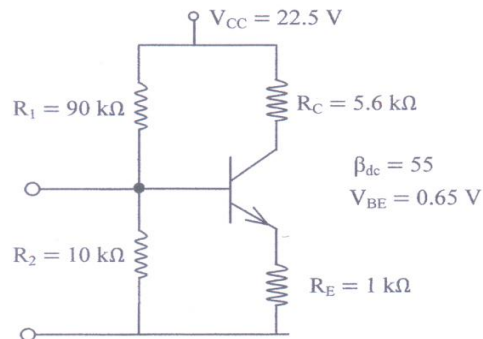1. Answer any **five** questions from the following: 2×5 = 10
- Define PIV in connection with a diode rectifier.
 - What is a clipping circuit?
 - Find the value of the current limiting resistance R_s , if a $\frac{1}{4}$ watt, 5.6 volt zener diode is connected to a 12 V supply.
 - What are the factors that affect the bias stability of a transistor?
 - What is thermal runaway in connection with transistor biasing?
 - Name the four feedback topologies.
 - What are the Barkhausen Criterion of oscillation?
 - What is Darlington connection?

Answer any six questions from the following5×6 = 30

- Explain how the dc output voltage of a full wave rectifier is improved when a capacitor filter is used. 3
 - Explain the significance of percentage voltage regulation. 2
- Using h -parameter model of a transistor amplifier, derive expressions for current gain and input impedance in CE-mode without considering the resistance of the source. $2\frac{1}{2} + 2\frac{1}{2}$
- Find the Q-point (V_{CE} , I_C) of the following emitter-bias circuit 5



- | | |
|--|-------------------------------|
| 5. (a) Draw the circuit diagram of a two-stage RC-coupled amplifier. | 2 |
| (b) Derive an expression of voltage gain in the mid frequency range. | 3 |
| 6. (a) Explain with the help of a block diagram the working principle of a feedback amplifier. Find out an expression of voltage gain with feedback. | 1+2 |
| (b) What are the advantages of negative feedback? | 2 |
| 7. (a) Draw the circuit diagram of a class-B push-pull amplifier. | 2 |
| (b) Explain its working principle. | 3 |
| 8. (a) Draw the circuit diagram of a RC phase shift oscillator. | 2 |
| (b) How is oscillation produced in this circuit? | 1 |
| (c) Derive the condition of sustained oscillation. | 2 |
| 9. (a) Draw a neat sketch of an emitter follower. | 1 |
| (b) Why is it so called? | 1 |
| (c) Write down the expressions for input resistance and voltage gain. | $1\frac{1}{2} + 1\frac{1}{2}$ |
| 10.(a) Explain the operation of an enhancement type MOSFET. | 3 |
| (b) What is the difference between enhancement type and depletion type MOSFET? | 2 |

—x—